

Attempt any four questions. [4 Q. x 4 marks = 16 marks]

1. For the circuit shown in figure 1, find the equivalent resistance. All resistors are $10\ \Omega$.

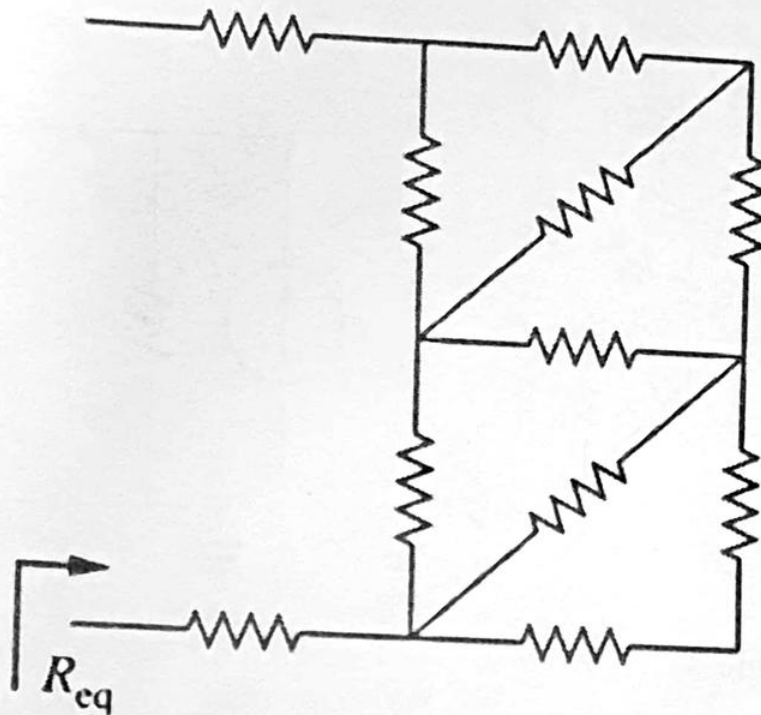


Figure 1

2. Determine v_o in the circuit of Figure-2 using the **Superposition Theorem**.

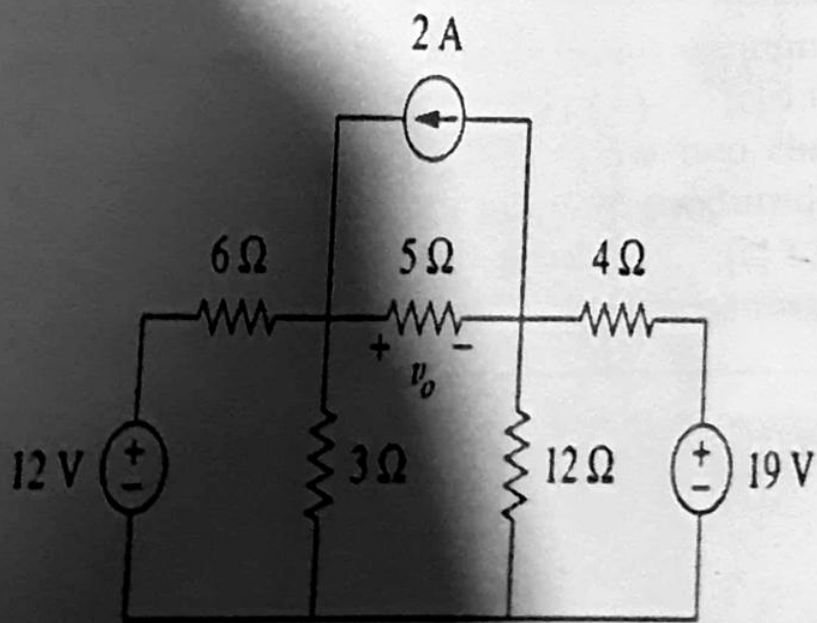


Figure-2

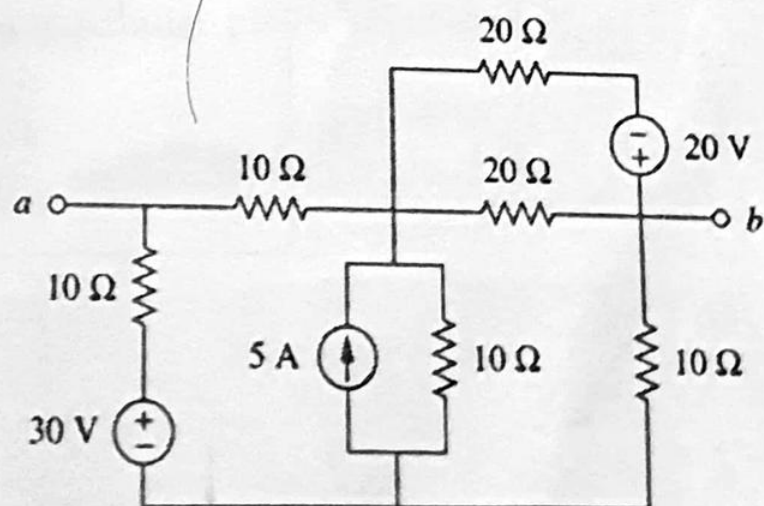


Figure 3

3. For the circuit in Figure 3, find the **Norton equivalent** between terminals a and b.

4. For the Figure 4:

- Determine I .
- Calculate I_4 .
- Find I_6 .
- Find I_{10} .
- Determine the total resistance across the 12V battery.

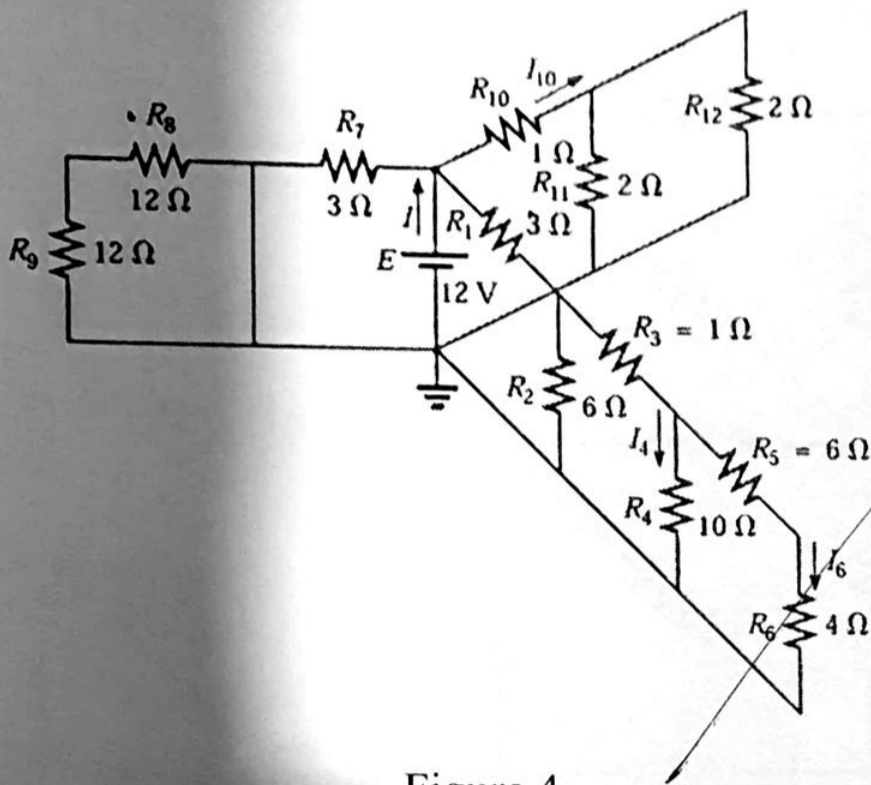


Figure 4

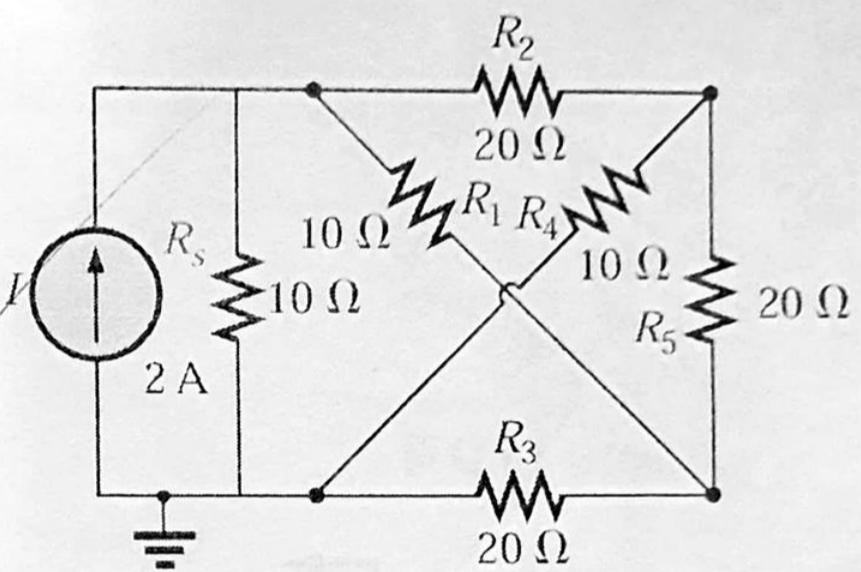


Figure 5

- Determine the current through the source resistor R_s of network of figure 5 using either **mesh** or **nodal analysis**. Discuss why you chose one method over the other.
- Obtain the **Thevenin Equivalent** Circuits at terminals a-b of the circuit in Figure 6.

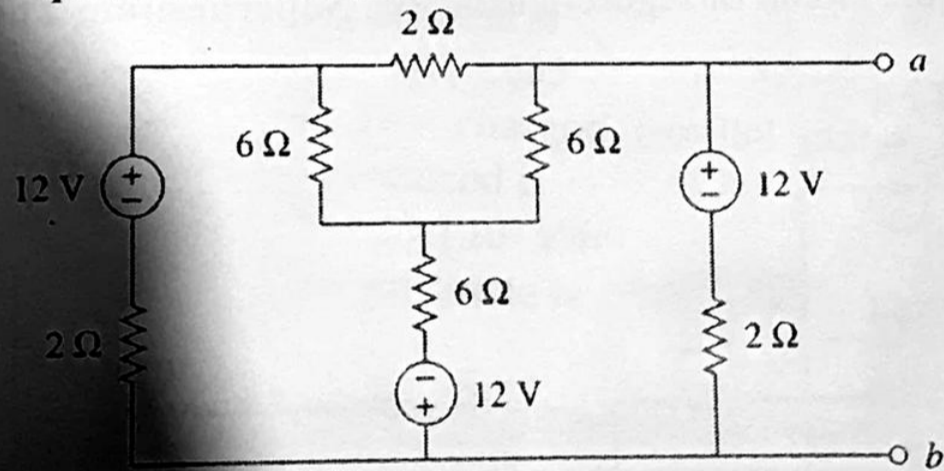


Figure 6